

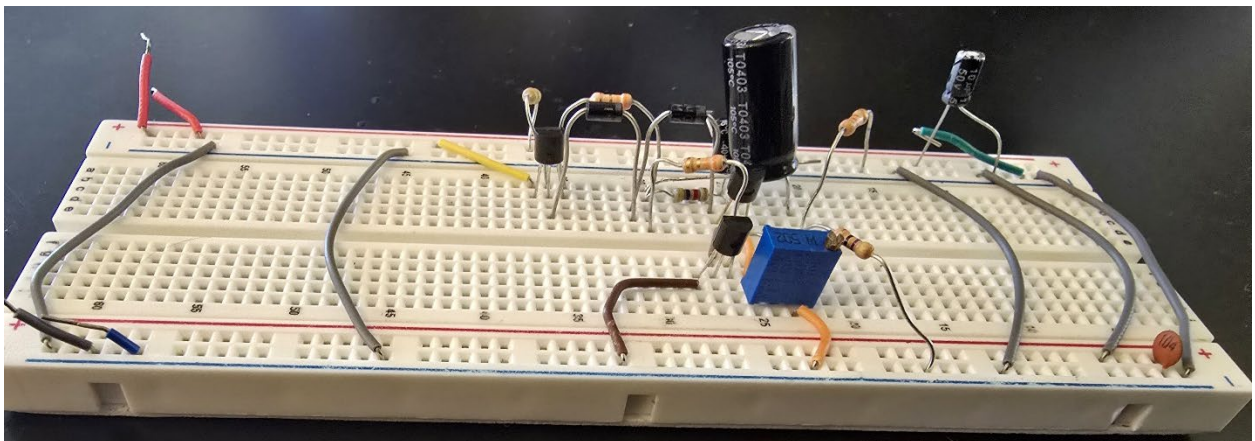
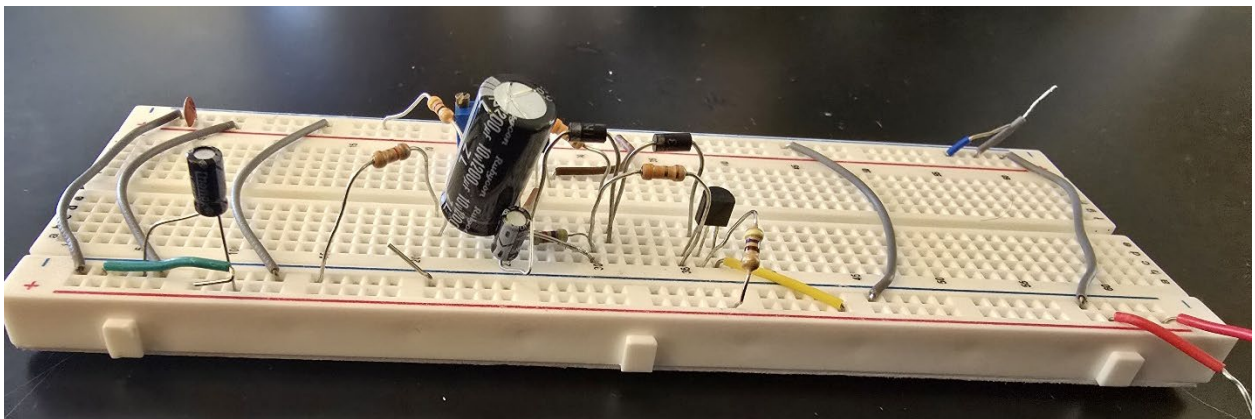


University of Arizona
Electrical & Computer Engineering
ECE 351C
Electronic Circuits
Dr. Hetherington
Class Project: Audio Amplifier
Breadboard Results
Jose Salinas Meza

Breadboard Pictures

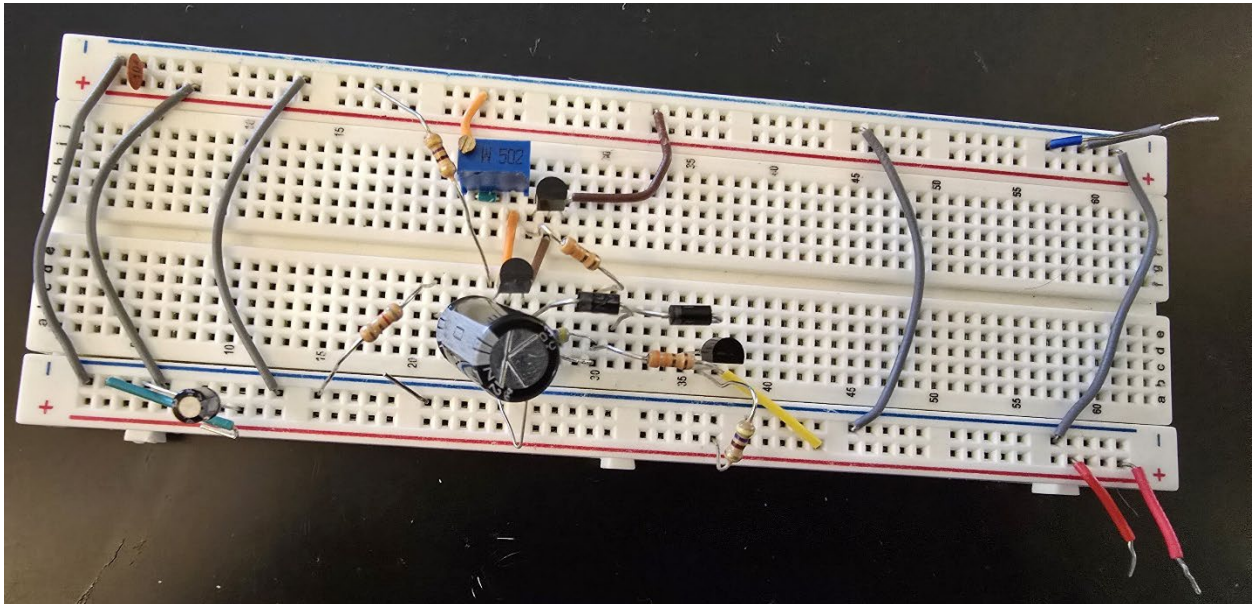

Sinewave Measurement 400mV pk-pk at 1Khz

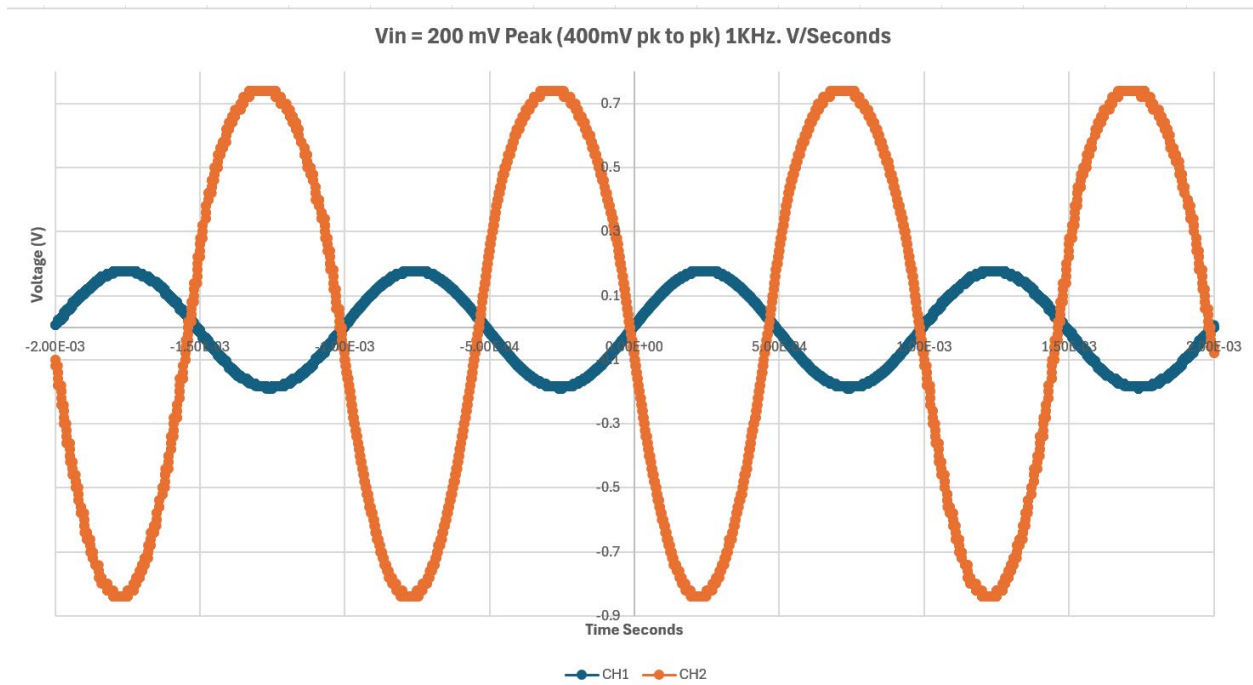


| Measurement | | |
|-------------|-----------|------------|
| | CH1 (Vin) | CH2 (Vout) |
| Max | 0.18 | 0.74 |
| Min | -0.19 | -0.84 |

| Gain Calculation | | |
|--------------------|-------|--------|
| | V/V | DB |
| Vout(Max)/Vin(Min) | -3.85 | -11.72 |
| Vout(Min)/Vin(Max) | -4.77 | -13.58 |

| Average Gain Calculation | | | |
|--------------------------|---------|----------|---------|
| | V pk-pk | Gain V/V | Gain dB |
| CH1 | 0.37 | 4.29 | 12.7 |
| CH2 | 1.58 | | |

Sinewave Measurement 1.2V pk-pk at 1Khz

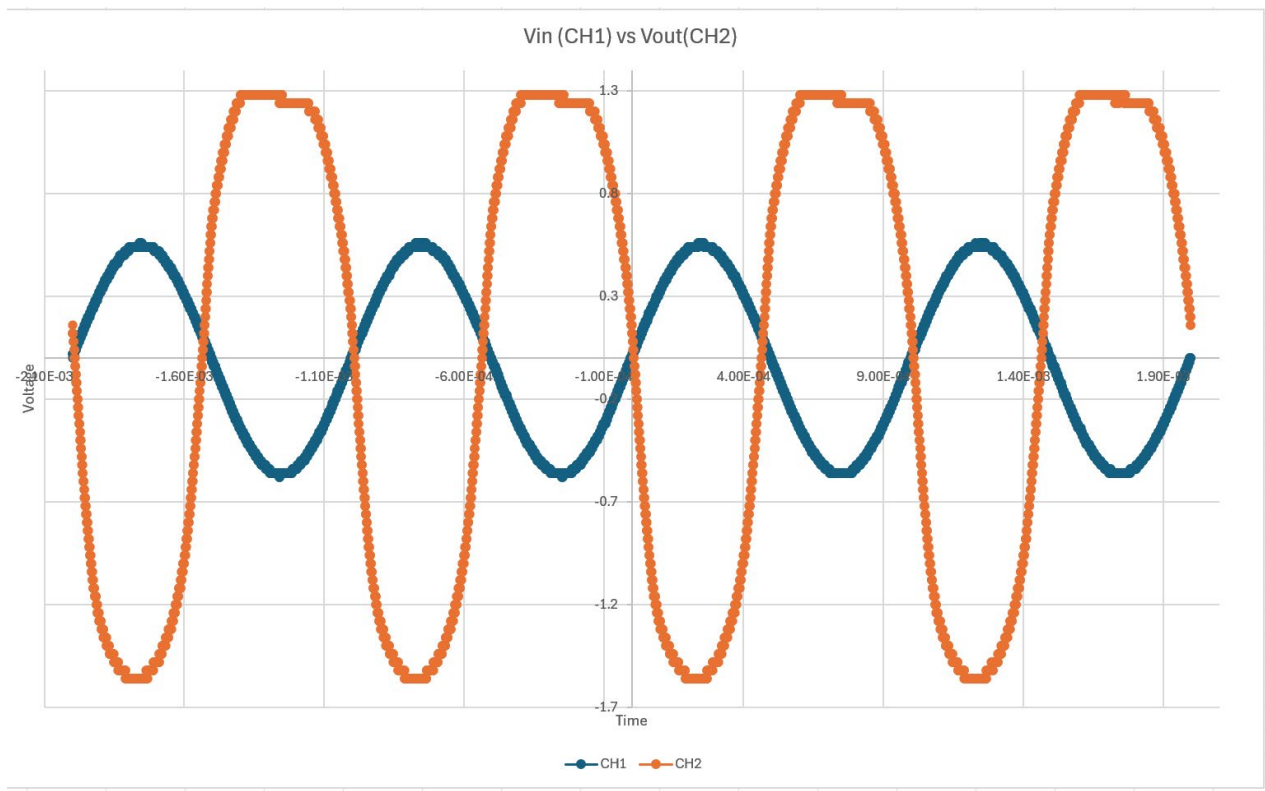

| Measurement | | |
|-------------|-----------|------------|
| | CH1 (Vin) | CH2 (Vout) |
| Max | 0.56 | 1.28 |
| Min | 0.58 | -1.56 |

| Gain Calculation | | |
|--------------------|-------|-------|
| | V/V | DB |
| Vout(Max)/Vin(Min) | -2.21 | -6.88 |
| Vout(Min)/Vin(Max) | -2.79 | -8.90 |

| Total Gain Calculation | | | |
|------------------------|---------|----------|---------|
| | V pk-pk | Gain V/V | Gain dB |
| CH1 | 1.14 | 2.49 | 7.9 |
| CH2 | 2.84 | | |

Power to Speaker Calculation

For a 500mAh Battery, the estimated lifetime is 4.2 Hours of playing music.

| Vin (mV) | Vout (V) | VoutRMS (V) | I RMS (mA) |
|-----------------------|----------|----------------------|------------|
| 900 | 2.76 | 0.98 | 121.98 |
| Power to Speaker (mW) | | Battery Life (Hours) | |
| 119.03 | | 4.2 | |

AC Sweep 400mV pk – pk

